
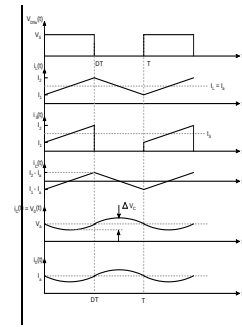


Buck converter

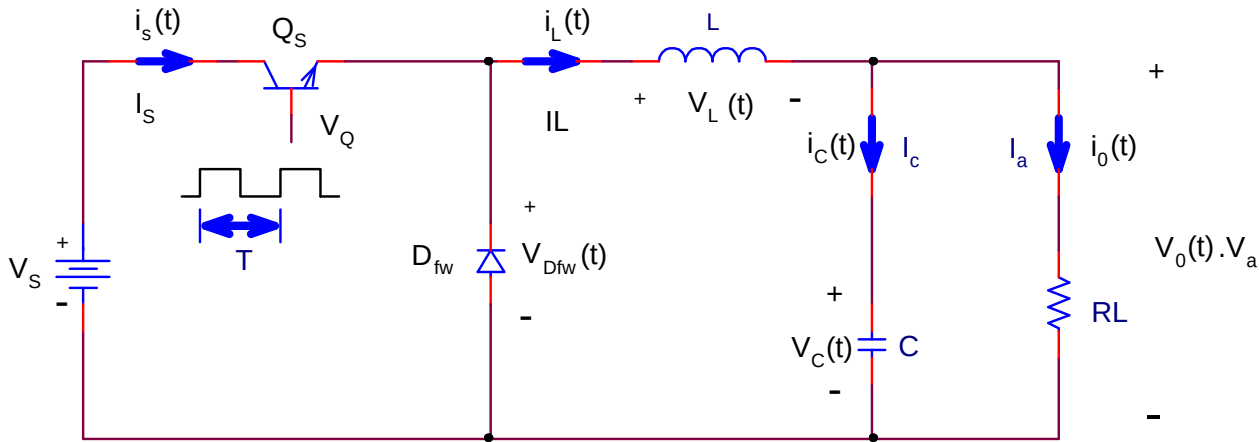


- The output voltage is smaller than the input voltage
- Same polarity



Buck converter

Continuous mode

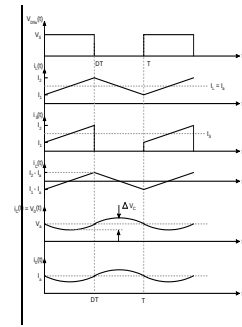


- *MODE 1* ($0 < t < t_{on}$)

$$v_L(t) = L \frac{di}{dt} ,$$

$$V_s - V_a = L \frac{I_2 - I_1}{t_{on}} = L \frac{\Delta I}{t_{on}} ,$$
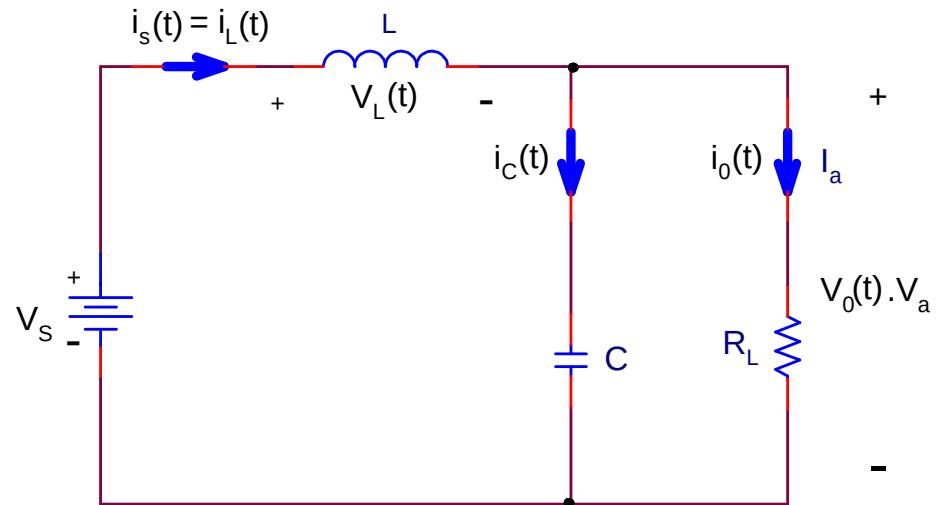
$$t_{on} = \frac{L \Delta I}{(V_s - V_a)} .$$



Buck converter

Continuous mode



- *MODE 2* ($t_{on} < t < T$)

$$-V_a = L \frac{I_1 - I_2}{t_{off}},$$

$$V_a = L \frac{\Delta I}{t_{off}}.$$



$$t_{off} = \frac{L \Delta I}{V_a},$$

$$\Delta I = \frac{V_a t_{off}}{L}.$$

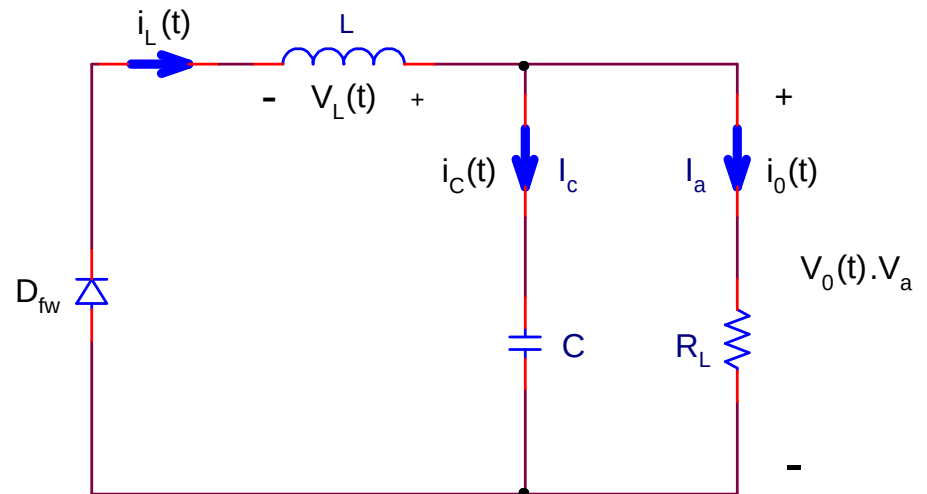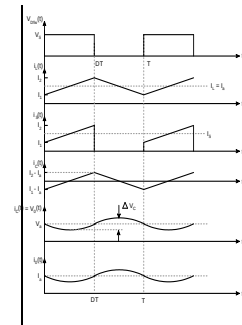


Buck converter

Continuous mode

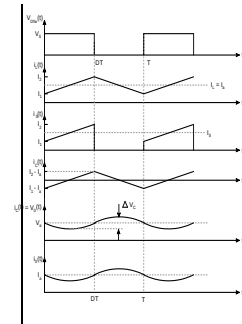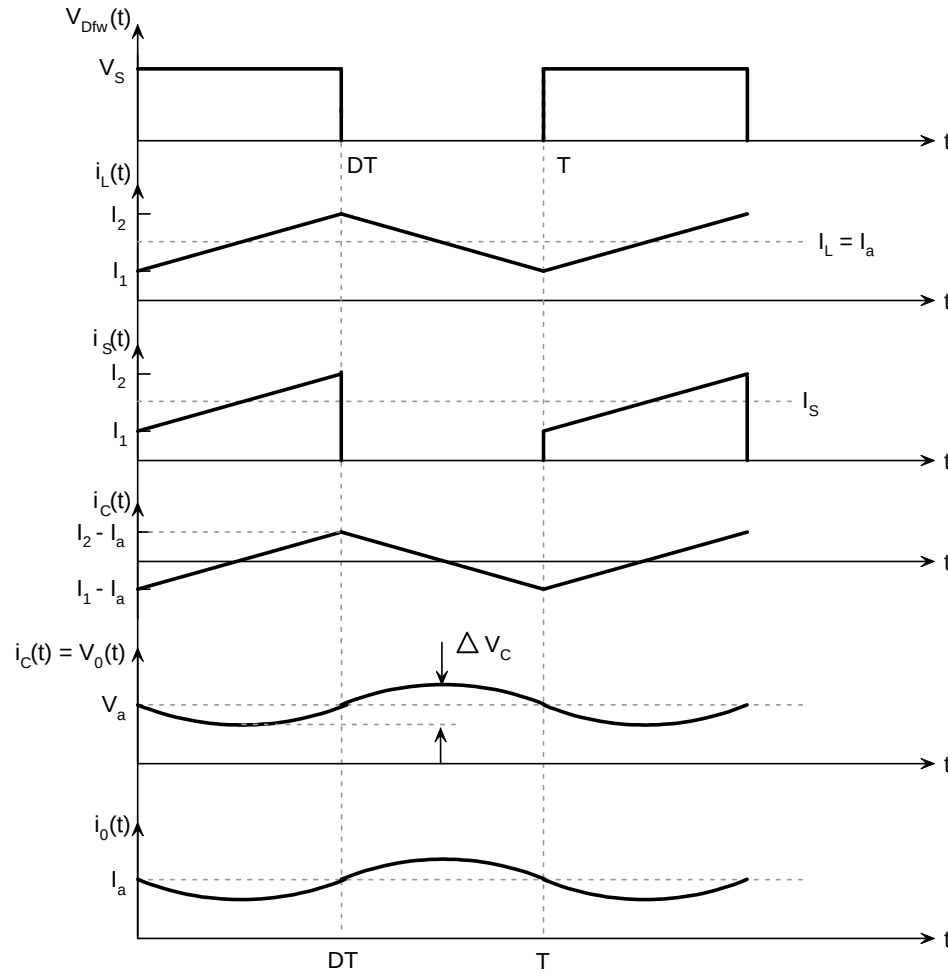

Buck converter

Continuous mode

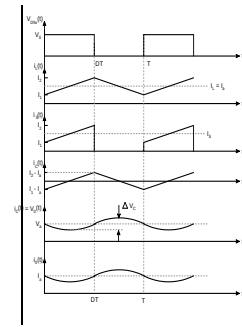

- Voltage conversion ratio


$$\Delta I = \frac{(V_s - V_a) t_{on}}{L} = \frac{V_a t_{off}}{L} .$$

$$(V_s - V_a) DT = V_a (1 - D) T$$

$$V_a = \frac{V_s DT}{T} = V_s D .$$

Buck converter

Continuous mode

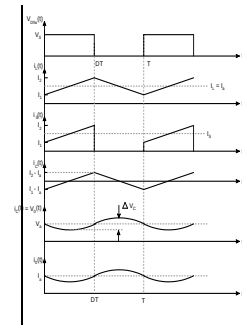


- Inductor ripple current

$$\begin{aligned} T &= \frac{1}{f_s} = t_{on} + t_{off} \\ &= \frac{L \Delta I}{V_s - V_a} + \frac{L \Delta I}{V_a} = \frac{L V_s \Delta I}{V_a (V_s - V_a)} \\ \Delta I &= \frac{V_a (V_s - V_a) T}{L V_s} = \frac{D V_s (1 - D)}{f_s L} . \end{aligned}$$

Buck converter

Continuous mode

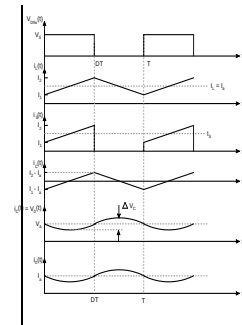

- Capacitor current
 - The average capacitor current I_c is zero

$$i_L = i_c + i_o$$


$$\Delta i_L = \Delta i_c + \Delta i_o \quad \square \quad \Delta i_c$$

$$\frac{t_{on}}{2} + \frac{t_{off}}{2} = \frac{T}{2}$$

$$I_c = \frac{\Delta I}{4} .$$

Buck converter

Continuous mode

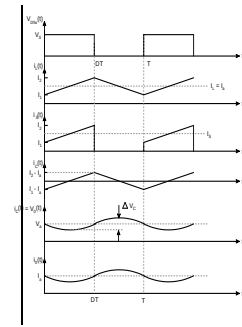

- Capacitor voltage

- The average capacitor voltage is V_a

$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^{\frac{T}{2}} i_c(t) dt$$


$$\Delta v_c = v_c(t) - v_c(0) = \frac{1}{C} \int_0^{\frac{T}{2}} \frac{\Delta I}{4} dt = \frac{T \Delta I}{8C} = \frac{\Delta I}{8 f_s C}$$

$$\Delta v_c = \frac{DV_s(1-D)}{f_s L} \cdot \frac{1}{8 f_s C} = \frac{V_s D(1-D)}{8 f_s^2 LC} .$$

Buck converter

Continuous mode

- Efficiency

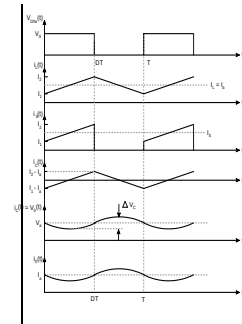


$$P_{loss} = P_{Q_s} + P_{D_{fw}} = I_o \left(\frac{t_{on}}{T} \right) V_{cesat} + I_o \left(1 - \frac{t_{on}}{T} \right) V_{D_{fw}}$$

$$\eta = \frac{P_{out}}{(P_{out} + P_{loss})} = \frac{V_a}{(V_a + D V_{cesat} + (1-D)V_{D_{fw}})} .$$

Buck converter

Critical inductance

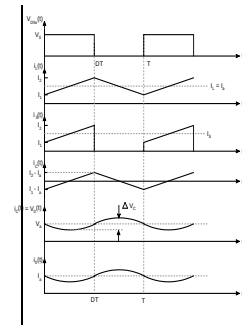

- If the load resistance is held constant and the inductance is reduced, the current ripple increases
- The value of L for which $i_L = 0$ at one and only one point per cycle is defined as the ***critical inductance*** L_c

Buck converter

Critical inductance

$$I_{Lp} = 2 I_L = \Delta I = \frac{(V_s - V_a) t_{on}}{L_c} = \frac{(V_s - V_a) D}{f_s L_c} .$$


$$P_{in} = V_s I_s = V_s I_L D$$

$$P_{out} = \frac{V_a^2}{R} ,$$

$$V_s I_L D = \frac{V_a^2}{R} .$$

$$I_L = \frac{\Delta I}{2} = \frac{(V_s - V_a) D}{2 f_s L_c} .$$

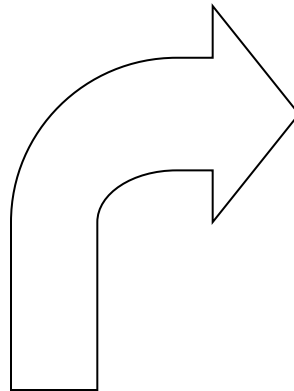
$$V_s \frac{(V_s - V_a) D^2}{2 f_s L_c} = \frac{V_a^2}{R} .$$



$$\frac{V_s^2 (1 - D) D^2}{2 f_s L_c} = \frac{V_a^2}{R} ,$$


$$\frac{(1 - D) D^2 V_s^2}{2 f_s L_c} = \frac{V_s^2 D^2}{R} .$$

$$L_c = \frac{R(1 - D)}{2 f_s} .$$

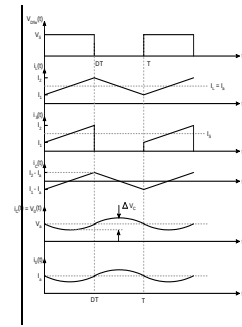

Buck converter

Critical load resistance

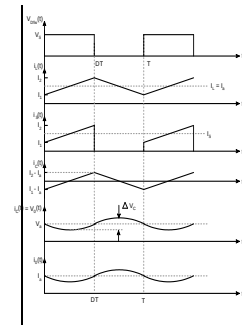


- If the inductance is held constant and the load resistance is increased, the inductor current decreases while keeping the ripple constant
- the buck converter will be operating in the discontinuous mode if the load resistance R is greater than its critical load resistance R_c

$$R_c = \frac{R_{nom}}{1 - D}$$

$$R_{nom} = 2 f_s L$$

Buck converter

Discontinuous conduction mode

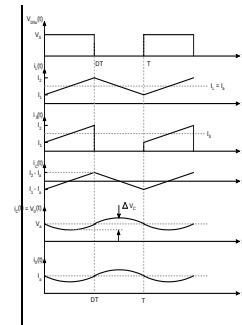

- If the load resistance is larger than the critical resistance


or

- If the inductance is smaller than the critical inductance


the buck converter will operate in the discontinuous conduction mode

Buck converter


Discontinuous conduction mode

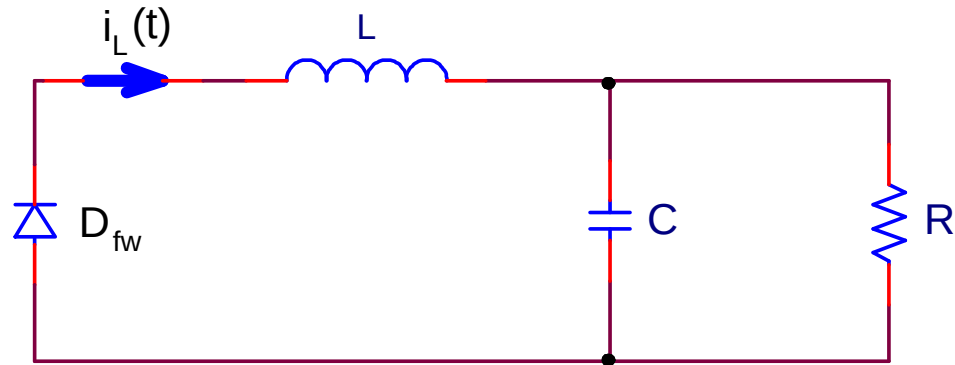

(a) $t_{on} < t \leq t_2$


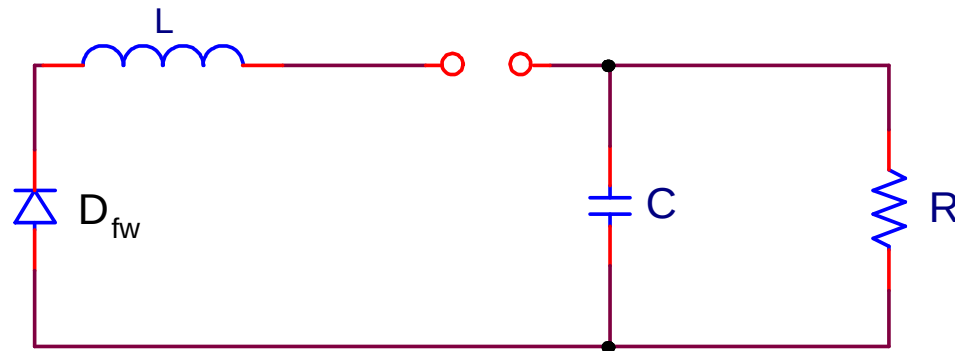


(a) $t_2 < t \leq T$

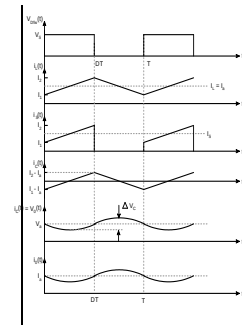

Buck converter

Discontinuous conduction mode

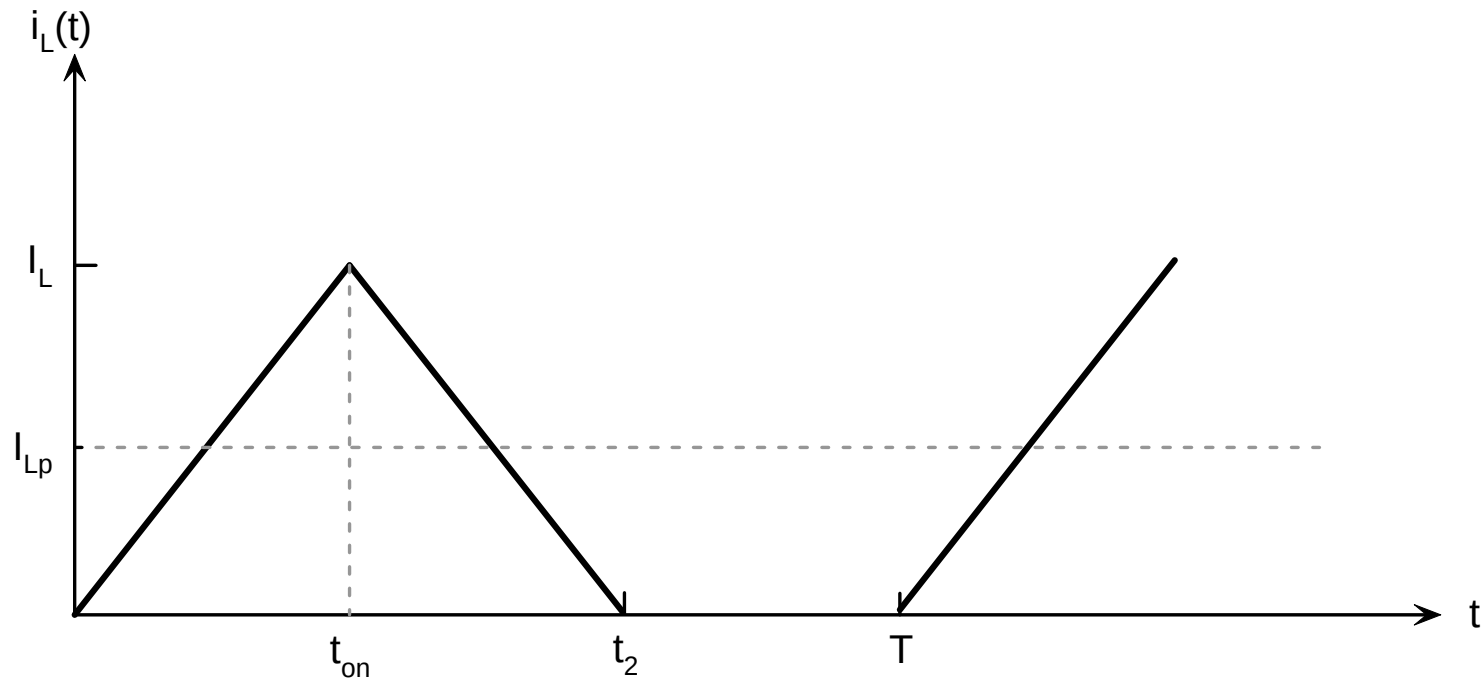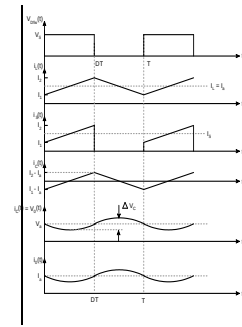

Buck converter

Discontinuous conduction mode

- Voltage conversion ratio

$$(V_s - V_a) t_{on} f_s - V_a (t_2 - t_{on}) f_s = 0 .$$

$$\frac{I_{Lp} t_2 f_s}{2} = \frac{V_a}{R} .$$

$$(V_s - V_a) = L \frac{I_{Lp}}{t_{on}} .$$

$$V_s t_{on} f_s - V_a t_2 f_s = 0 .$$


Substituting $t_2 f_s$ and I_{Lp} into the above equation,

$$V_a^2 + V_a V_s \frac{D^2 L_c}{(1-D)L} - V_s^2 \frac{D^2 L_c}{(1-D)L} = 0 .$$

This is a quadratic equation


$$\frac{V_a}{V_s} = \frac{D \left[\sqrt{\frac{4L(1-D)}{L_c} + D^2} - D \right]}{2L(1-D)} L_c$$
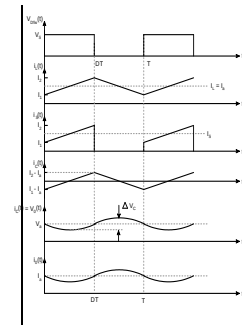
$$\frac{V_a}{V_s} = \frac{2}{1 + \sqrt{1 + \frac{4L(1-D)}{D^2 L_c}}} ; L < L_c$$




Buck converter

Voltage conversion ratio

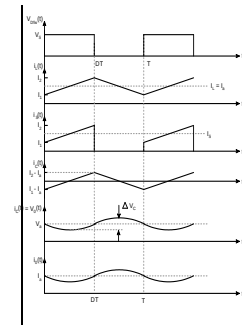


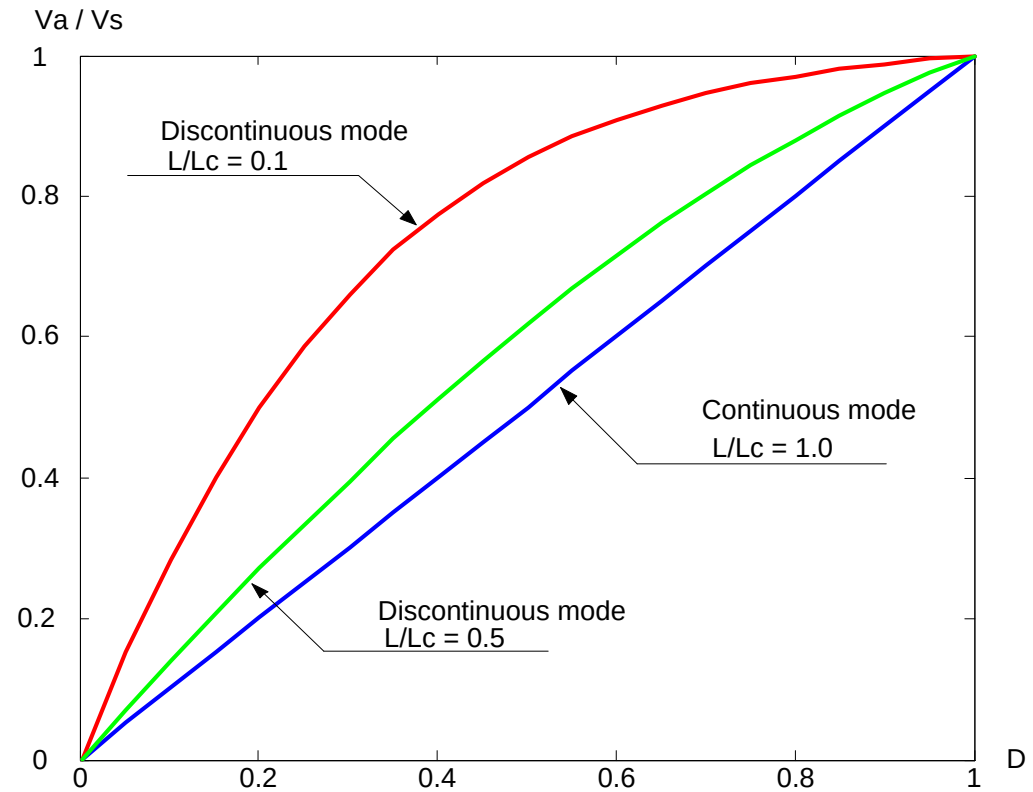- Continuous mode
 - Linear
- Discontinuous mode
 - Non linear




Buck converter

Discharge time in the discontinuous mode

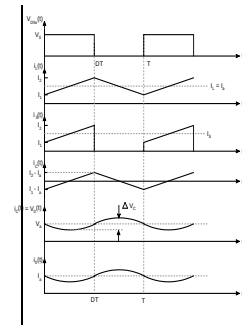


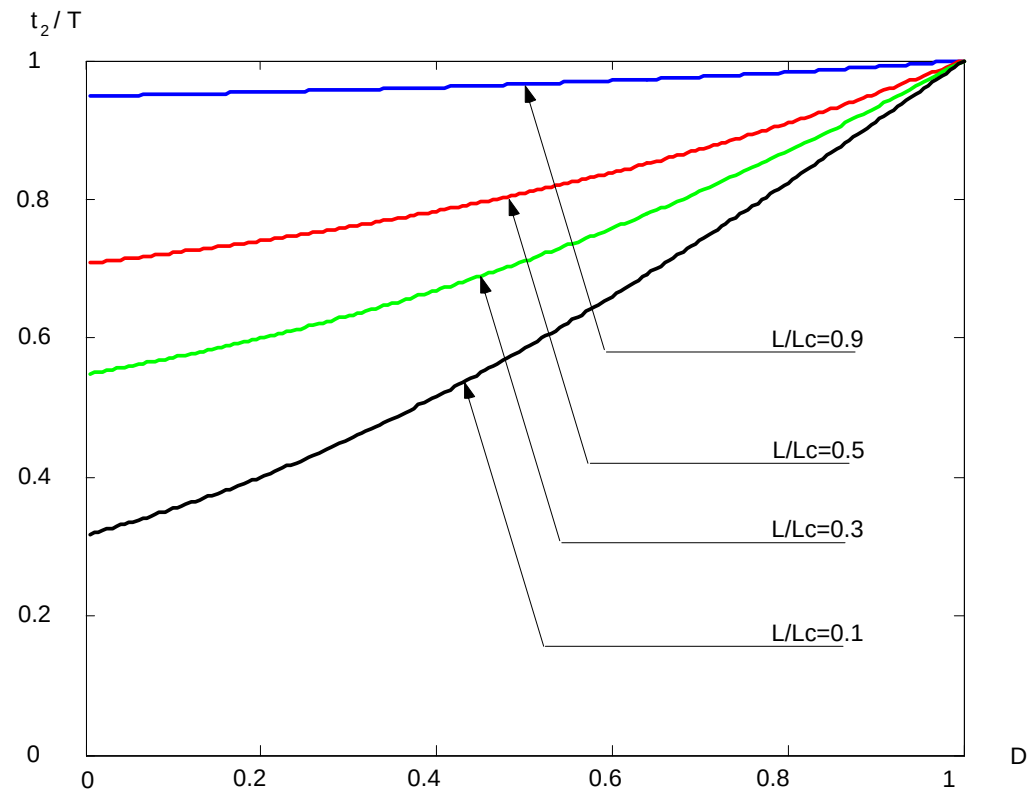- Decreasing the inductance
 - Forces the converter deeper in the discontinuous mode
 - Decreases the discharge time
 - Reduces the losses on the diode
 - Increases the stresses




Buck converter

Switching waveforms

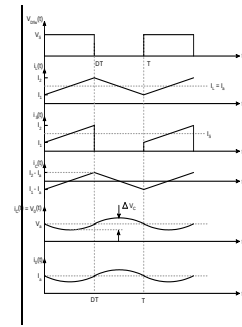


• Continuous mode

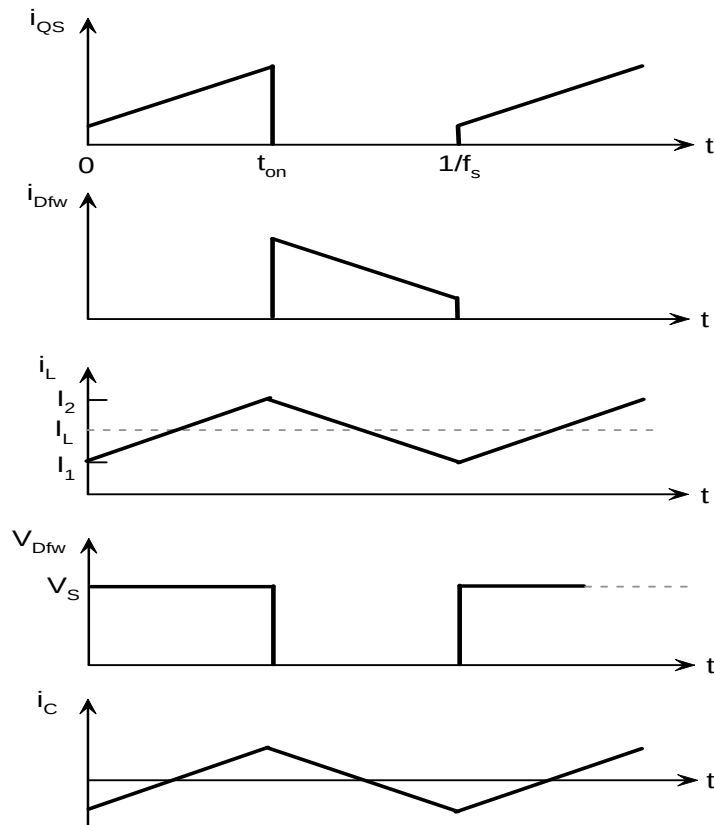


(a)

• Discontinuous mode

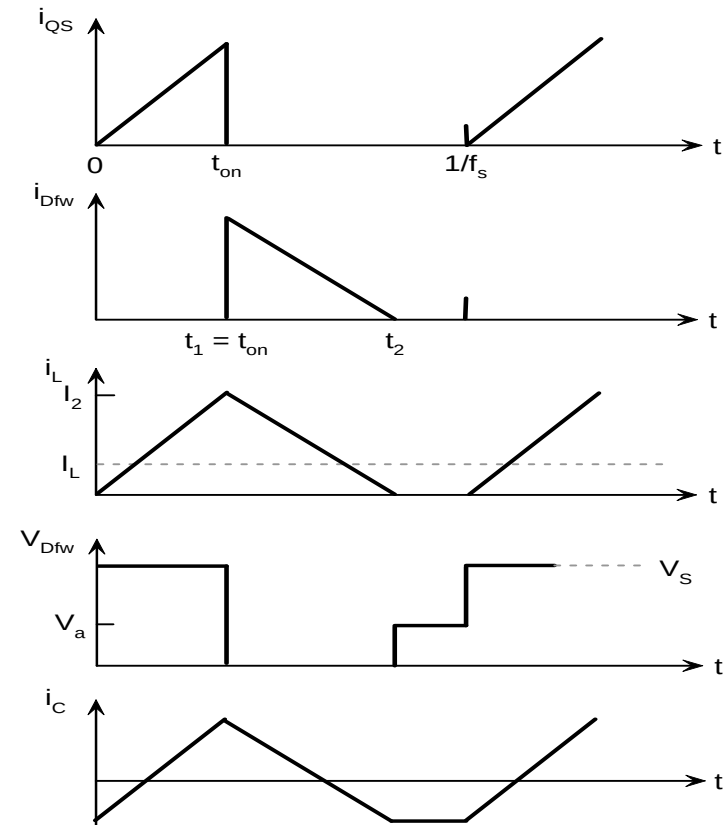

(b)


Buck converter

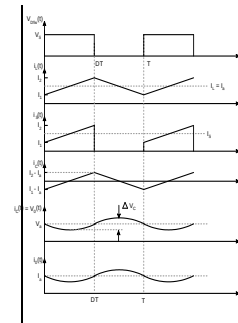

- Design the switching converter to operate either in the continuous or the discontinuous mode
- If the load of a buck converter is suddenly removed, the output voltage of an open-loop buck converter will rise to the same level as the input voltage
- The advantages of the buck converter are its ability to easily control output voltages and currents during turn-on and turn-off and under fault conditions

Buck converter


Example 2-1

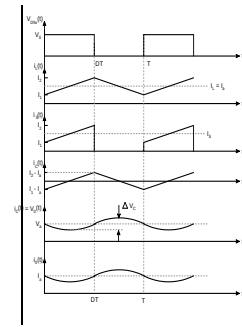

- The buck converter with a bipolar switching transistor, as shown in Figure 2.1, has an input voltage of 10 V. The switching frequency is 1 kHz. The load requires an average voltage of 5 V with a maximum ripple voltage of 20 mV. The maximum ripple current of the output inductor is 0.2 A. Determine: (a) the duty cycle, (b) the output inductance, (c) the output capacitance, and (d) the output capacitance if the switching frequency is increased to 10 kHz.

Buck converter

Example 2-1

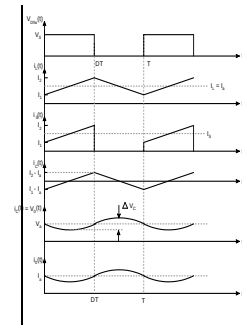

$$D = \frac{V_a}{V_s} = \frac{5}{10} = 0.5 \text{ .}$$


$$L = \frac{DV_s(1-D)}{f_s \Delta I} = \frac{0.5(10)(0.5)}{1000(0.2)} = 0.0125 \text{ H} = 12.5 \text{ mH} \text{ .}$$

$$C = \frac{V_s D(1-D)}{8 f_s^2 L \Delta V_a} = \frac{10(0.5)(0.5)}{8(1000)^2 0.0125(0.02)} = 1250 \text{ } \mu\text{F} \text{ .}$$

$$L = \frac{0.5(10)(0.5)}{10000(0.2)} = 0.00125 \text{ H} \text{ .}$$

$$C = \frac{10(0.5)(0.5)}{8(10000)^2 0.00125(0.02)} = 125 \text{ } \mu\text{F} \text{ .}$$

Synchronous Buck Converter


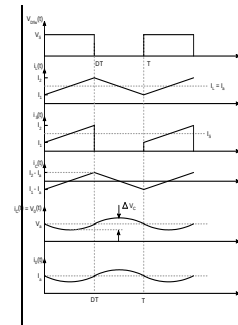


- When the output voltage of a buck converter is calculated, considering V_d yields:

$$V_a = DV_s - (1 - D)V_d$$



- It is possible to replace the Schottky diode by a power MOSFET, this is the buck synchronous converter
- SBC works only in the continuous conduction mode

Synchronous Buck Converter

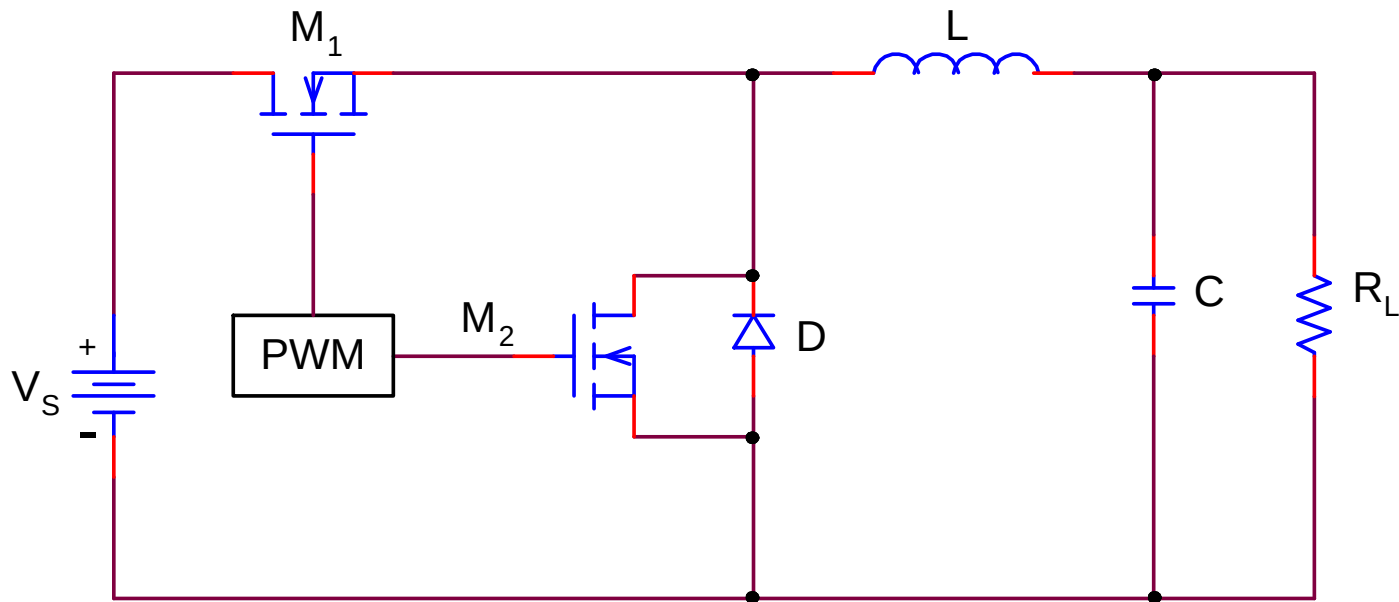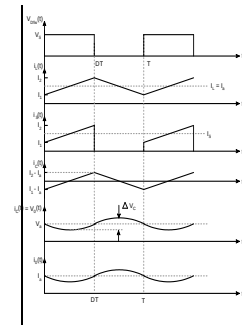


Ripple Steering

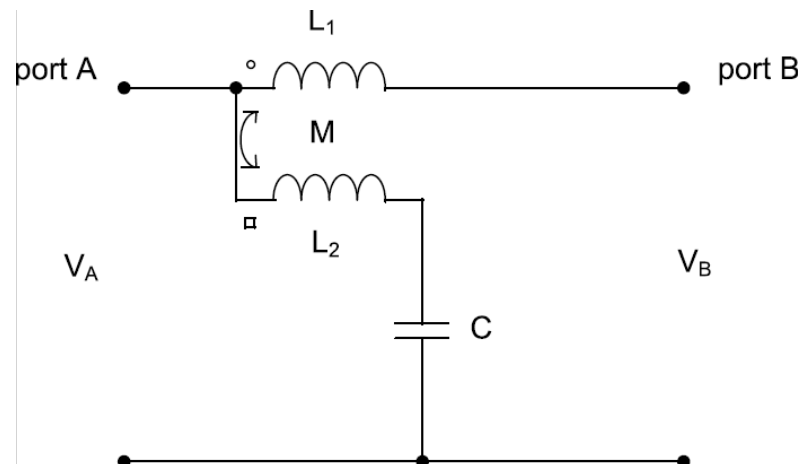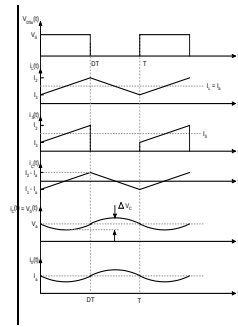- Replace the series inductor with a pair of coupled inductors and a DC blocking capacitor to reduce the current ripple flowing through the inductor.
- Objective is to remove or filter the AC ripple present at port A to produce a clean DC voltage at port B by re-directing or steering the ripple current to an auxiliary branch of L_2 and C .






Ripple Steering

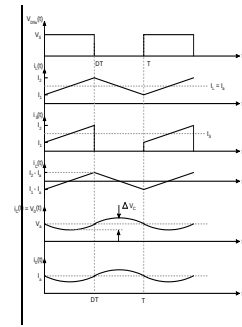

- Consider the case of a perfect coupling of L_1 and L_2 and $L_1=L_2$. Also, the dc blocking capacitance C is infinity.
- Using KVL, we have $V_A = V_{Aac} + V_{Adc}$
- Since the capacitance of C is infinity, its AC impedance is zero. Therefore, $V_C = V_{Adc}$.
- Thus, the voltage drop across L_2 is $V_{L2} = V_{Aac}$.
- For a perfect coupling of L_1 and L_2 , $V_{L1} = V_{L2} = V_{Aac}$.
- Hence, the out port B voltage is $V_B = V_{Adc}$.
- The output port B is a pure DC voltage since the ripple current has been steered to the auxiliary branch of L_2 and C .

Buck Converter with LC Branch

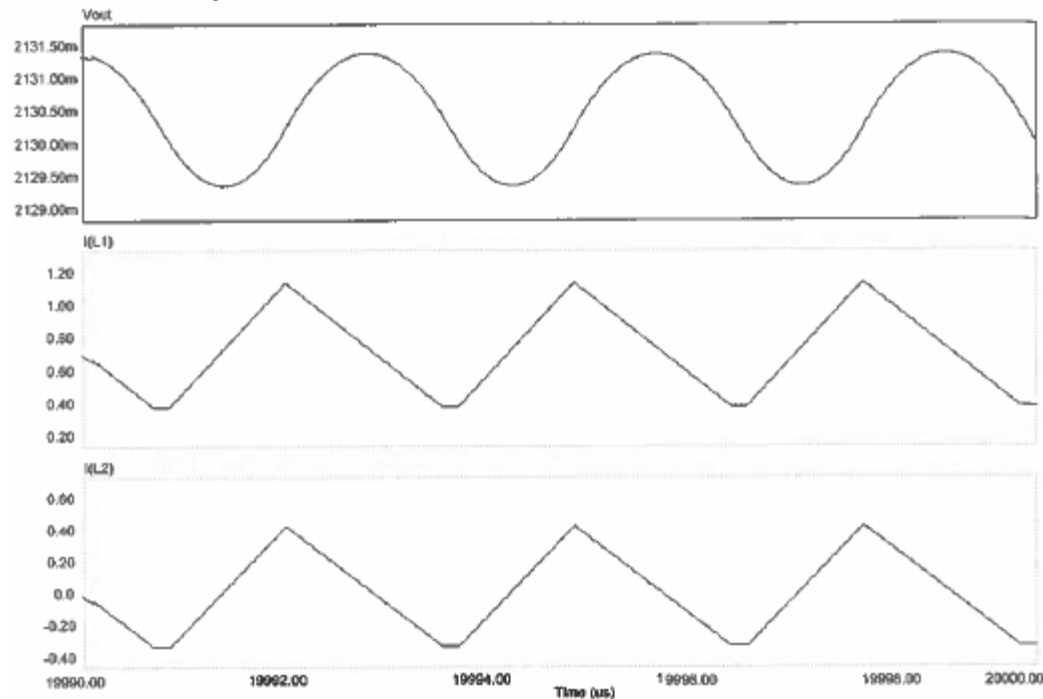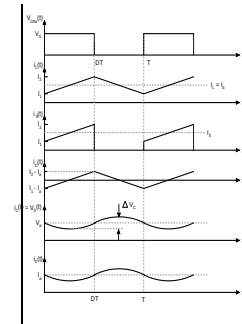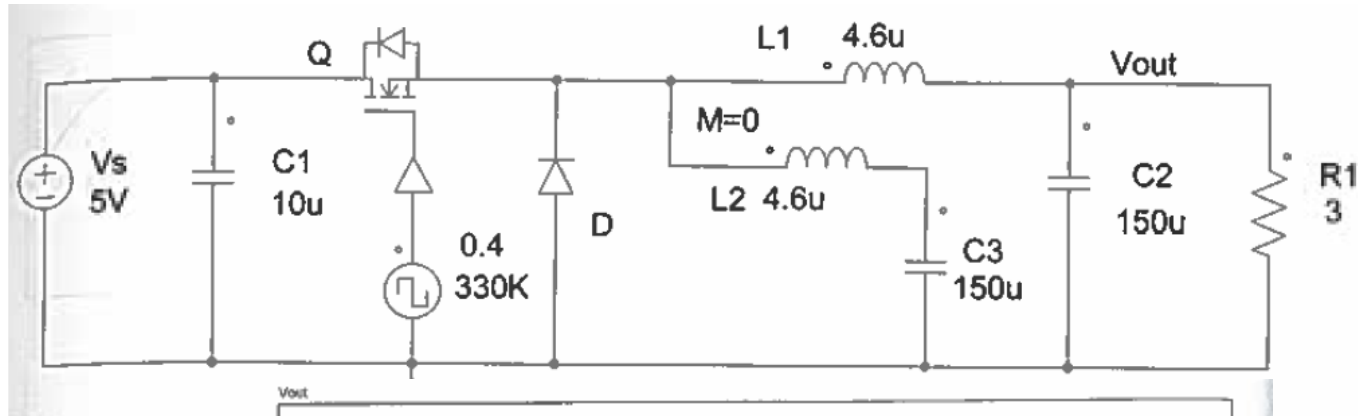

Buck Converter with Coupled L

